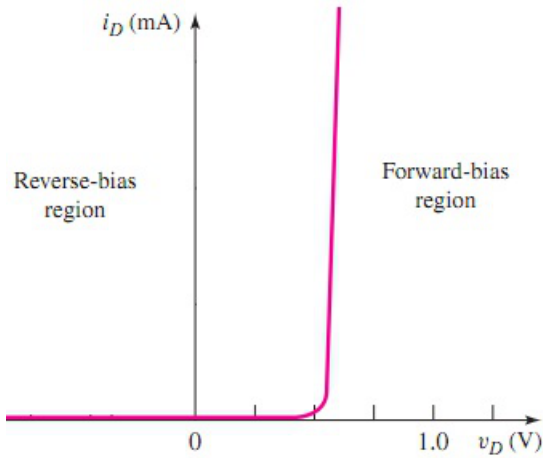


# Diode models and Diode Logic

Ang Man Shun

December 18, 2012

## 1 Diode DC Model - Shockley diode model



The Shockley diode model equation is

$$i_D = I_S \left[ e^{\frac{v_D}{nV_T}} - 1 \right] \quad v_D = nV_T \ln \left( \frac{i_D}{I_S} + 1 \right)$$

$V_D$  : Diode Voltage

$i_D$  : Diode Current

$I_S$  : Reverse-bias saturation current  $10^{-15} \sim 10^{-13} A$

$V_T$  : Thermal voltage  $V_T = \frac{kT}{q} \approx 26mV_{300K}$


$n$  : Ideality factor,  $n \in [1, 2]$

### 1.1 Diode block reverse current

$$i_D = 10^{-14} \left[ e^{\frac{V_D}{0.026}} - 1 \right] \begin{cases} \text{Forward} & V_D = 0.7V & i_D = 10^{-14} \left[ e^{\frac{0.7}{0.026}} - 1 \right] \approx 4.93mA \neq 0 \\ \text{Reverse} & V_D = -0.7V & i_D = 10^{-14} \left[ e^{\frac{-0.7}{0.026}} - 1 \right] \approx -10^{-14}A = 0 \end{cases}$$

So diode can be treated as a blocker of reverse current
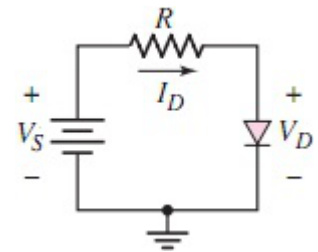
### 1.2 Standard Diode-Resistor DC circuit



$$\text{Standard equations of DR circuit} \begin{cases} V_S = i_D R + v_D \\ i_D = I_S \left[ e^{\frac{v_D}{nV_T}} - 1 \right] \end{cases}$$

$$\iff V_S = I_S R \left[ e^{\frac{v_D}{nV_T}} - 1 \right] + v_D \quad V_S = i_D R + V_T \ln \left( \frac{i_D}{I_S} + 1 \right)$$

Both equations are transcendental, can be solved by using special functions or numerical methods.

### 1.3 Diode DC Approximation

$$\text{When } v_D > 4V_T \approx 0.1V \quad i_D = I_S \left[ e^{\frac{v_D}{nV_T}} - 1 \right] \approx i_D = I_S e^{\frac{v_D}{nV_T}}$$

## 2 Diode AC Circuit

For AC circuit with  $V_{DQ} > 0.1V$

$$v_D = V_{DQ} + v_d$$

$$i_D = I_S e^{\frac{v_D}{V_T}} \rightarrow i_D = I_S e^{\frac{V_{DQ} + v_d}{V_T}}$$

$$i_D = \left( I_S e^{\frac{V_{DQ}}{V_T}} \right) e^{\frac{v_d}{V_T}}$$

$$\approx I_{DQ} \left( 1 + \frac{v_d}{V_T} \right)$$

$$= I_{DQ} + I_{DQ} \frac{v_d}{V_T}$$


$$= I_{DQ} + i_d$$

Thus

$$i_d = \frac{I_{DQ}}{V_T} v_d \quad i_d = g_d v_d \quad g_d = \frac{I_{DQ}}{V_T}$$


Or
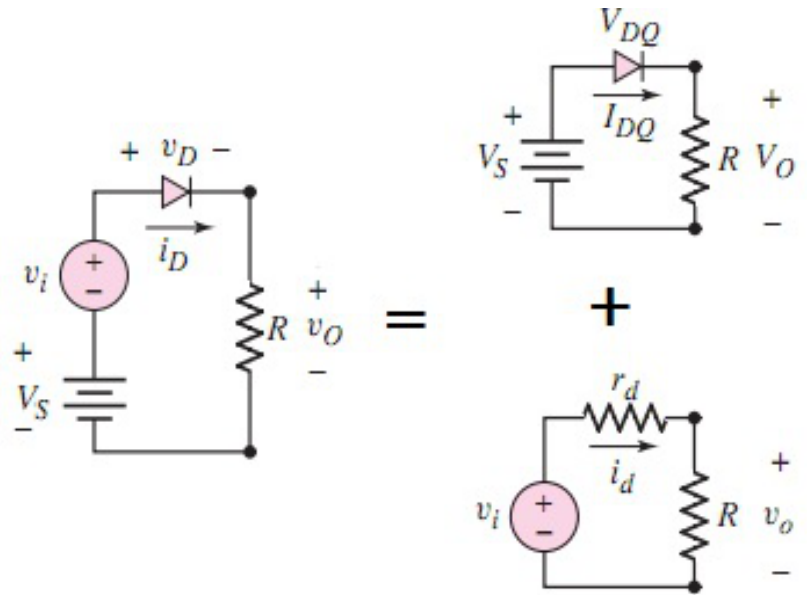
$$v_d = r_d i_d \quad r_d = \frac{1}{g_d} = \frac{V_T}{I_{DQ}}$$



(Principle of Superposition)



### 3 Diode-Resistor Logic

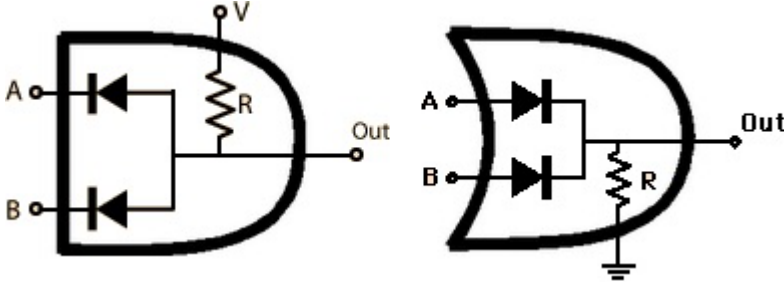

#### 3.1 OR Logic
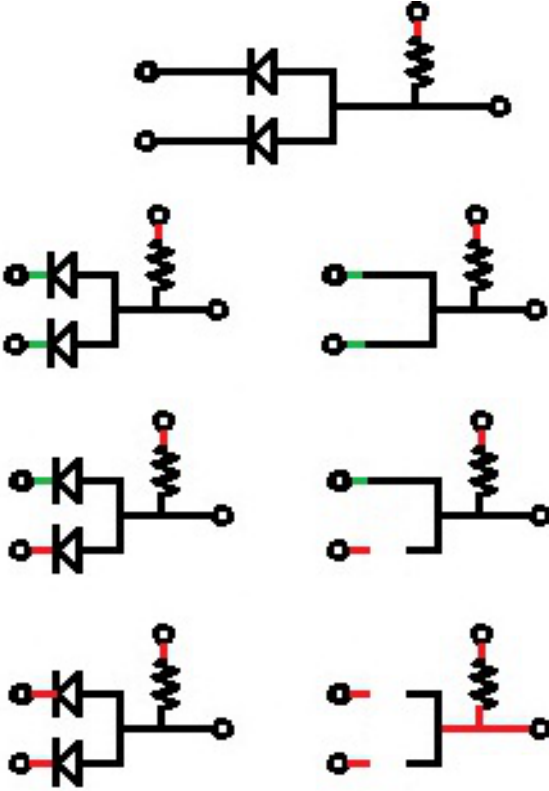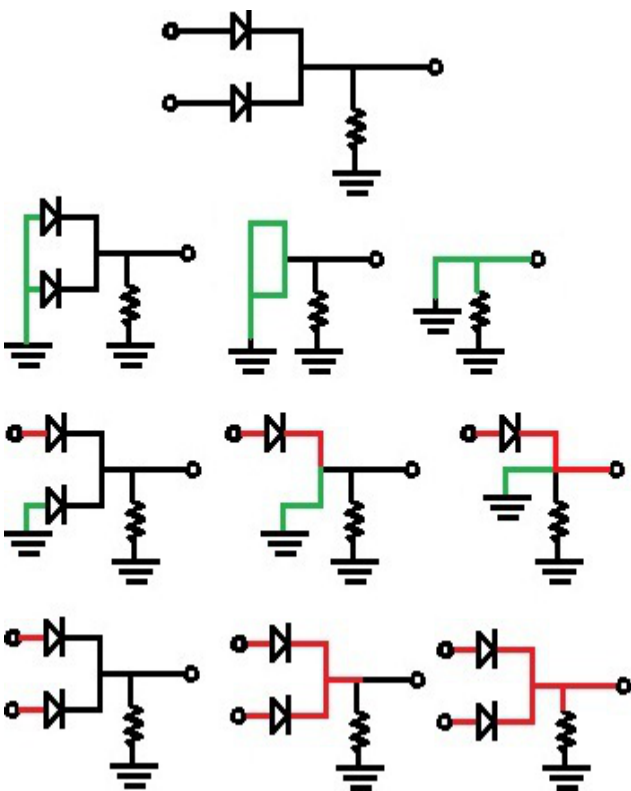
#### 3.2 And Logic

Red means logic high, 5V , Green means logic low, 0V



-END-