

# Operation Modes of BJT and MOSFET

## Cutoff, Active and Saturation

Ang Man Shun  
December 13, 2012

### Reference


Sedra and Smith *Microelectronic Circuit*

Neamen *Microelectronics*

## 1 BJT

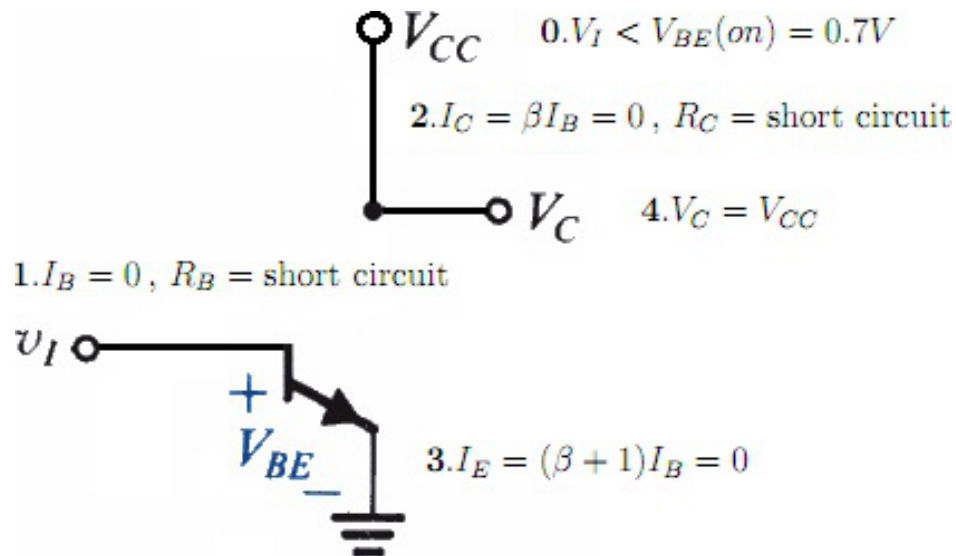
### 1.1 Cutoff Mode

- When  $V_I < V_{BE(on)}$ , it can not turn on the BE-Junction diode, the BJT is in cutoff mode


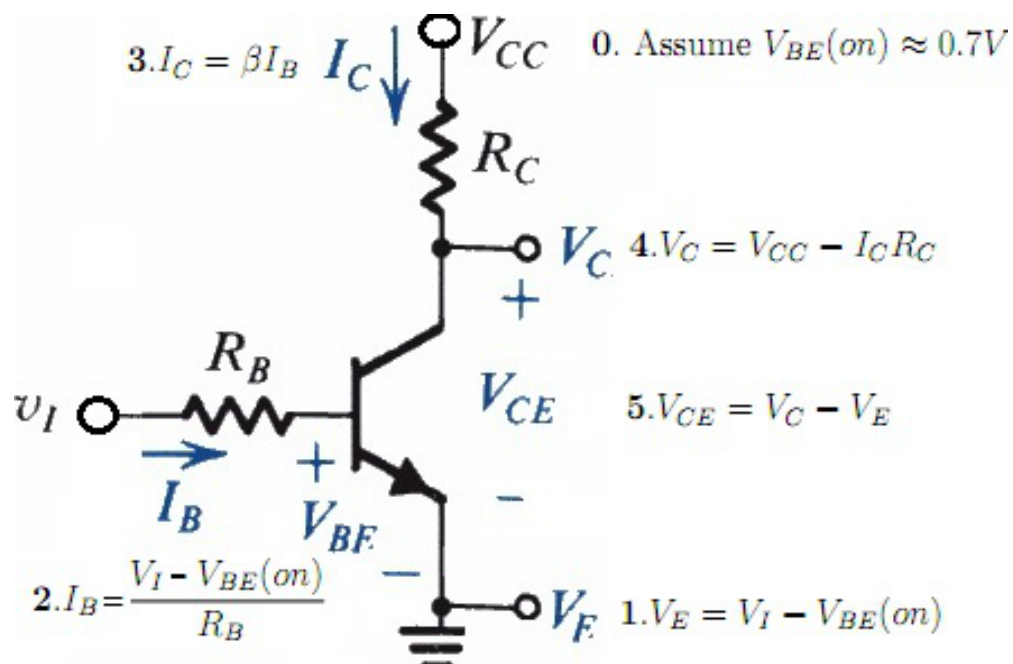
### 1.2 Forward Active Mode

- When  $V_I > V_{BE(on)}$ ,  $I_B \neq 0$  and  $V_{CE} > 0.2V$



### 1.3 Saturation Mode

Re-consider the  $V_C$  again

$$\begin{aligned}
 V_C &= V_{CC} - I_C R_C \\
 &= V_{CC} - \beta I_B R_C = V_{CC} - \beta R_C \left( \frac{V_I - V_{BE(on)}}{R_B} \right) \\
 &= \left( \underbrace{V_{CC} + \beta \frac{R_C}{R_B} V_{BE(on)}}_{Constant} \right) - \left( \underbrace{\beta \frac{R_C}{R_B}}_{Constant} \right) V_I \\
 &= A - B V_I
 \end{aligned}$$

If  $V_I$  increase,  $V_C$  decrease


Re-consider the  $V_{CE}$  again

$$\begin{aligned}
 V_{CE} &= V_C - V_E \\
 &= \left( \underbrace{V_{CC} + \beta \frac{R_C}{R_B} V_{BE(on)}}_{Constant} \right) - \left( \underbrace{\beta \frac{R_C}{R_B}}_{Constant} \right) V_I - [V_I - V_{BE(on)}] \\
 &= \left( \underbrace{V_{CC} + \left( \beta \frac{R_C}{R_B} + 1 \right) V_{BE(on)}}_{Constant} \right) - \left( \underbrace{\beta \frac{R_C}{R_B} - 1}_{Constant} \right) V_I \\
 &= A' - B' V_I
 \end{aligned}$$

If  $V_I$  increase,  $V_{CE}$  decrease

When  $V_{CE}$  drop down to a value that  $I_C$  is independent of  $I_B$ , the BJT is now working in saturation mode.

In saturation mode :

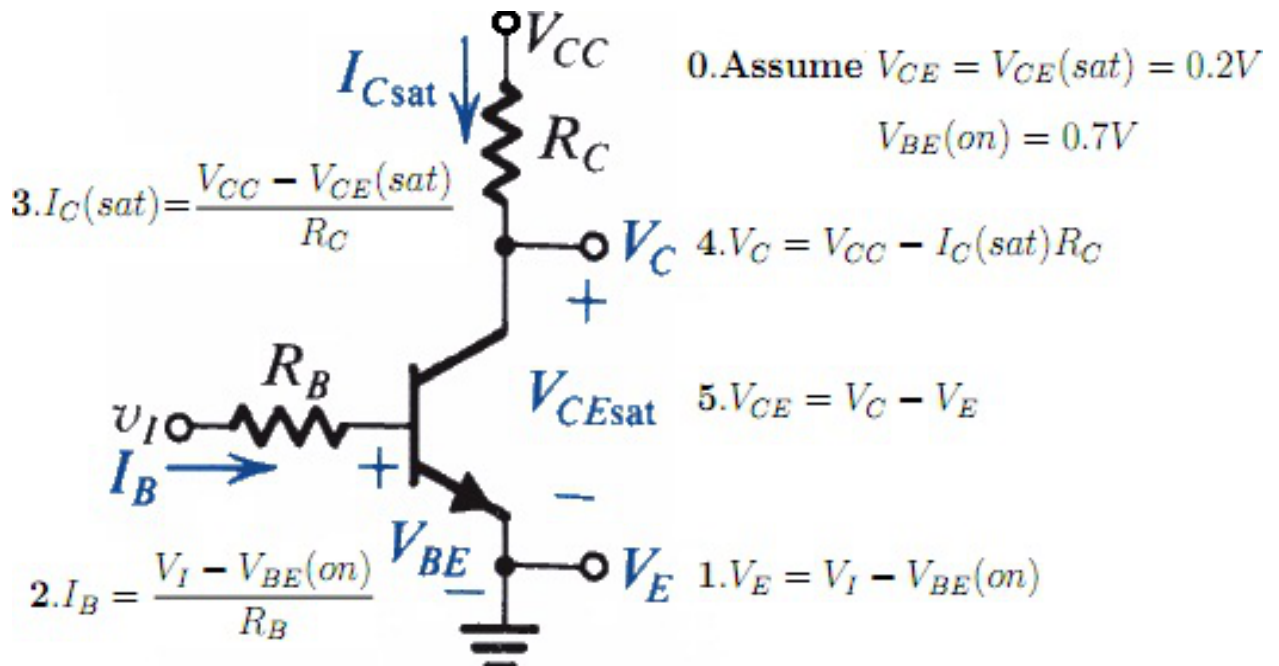

$V_{CE}$  in this case will be smaller than  $V_{CE}(sat) = 0.2V$  :

$$V_{CE} = V_C - V_E$$

$$= (V_{CC} - I_C(sat)R_C) - (V_I - V_{BE}(on))$$

$$= (V_{CC} + V_{BE}(on)) - V_I - I_C(sat)R_C$$

$$V_{CE} = (V_{CC} + V_{BE}(on)) - V_I - \frac{V_{CC} - V_{CE}(sat)}{R_C}R_C$$


$$V_{CE} = V_{CE}(sat) - \underbrace{\left( V_I - V_{BE}(on) \right)}_{>0}$$

$V_I > V_{BE}(on)$  , otherwise, cutoff mode ( contradiction ! ), thus  $V_I - V_{BE}(on) > 0$  , and thus

$$V_{CE} = V_{CE}(sat) - \underbrace{\left( V_I - V_{BE}(on) \right)}_{>0} < V_{CE}(sat)$$

$$V_{CE} < V_{CE}(sat) \approx 0.2V$$

## 2 MOSFET

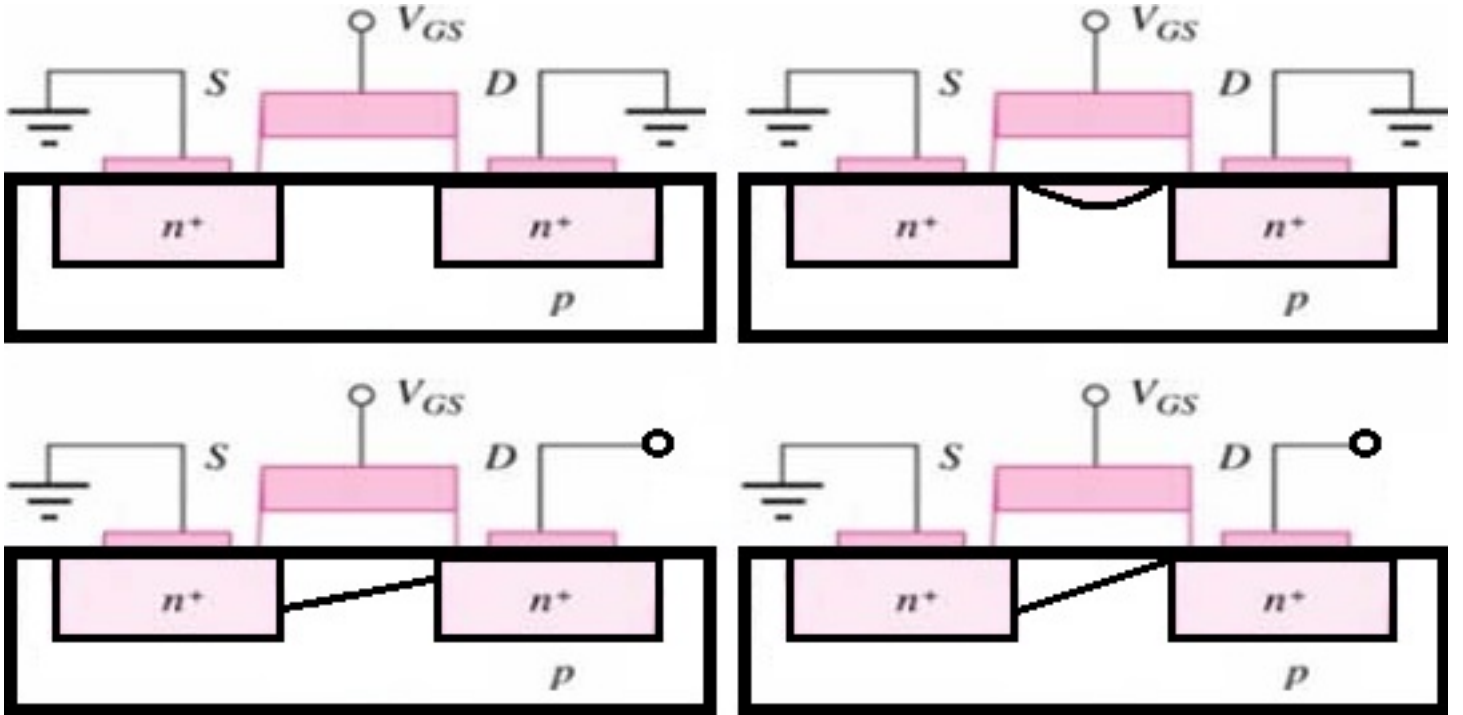

## 2.1 MOSFET Device

### 2.1.1 Cutoff

When  $V_{GS} = 0$ , the MOSFET is just like two back-to-back diode, no current, so cut off.

$$I_{DS} = 0$$

When  $V_{GS} > 0$  but  $V_{GS} < V_{TN}$ , since the MOSFET structure looks like a capacitor, there is some positive charge stored in the metal plate, while in the semiconductor, there is some negative charge. Since the  $V_{GS}$  is not large enough, so there is no “ $n$ -channel”, there is still no current.

### 2.1.2 Triode / Active

When  $V_{GS} > V_{TN}$ , there is enough voltage or E-field attraction to establish a  $n$ -channel in the semiconductor, so the 2 n-semiconductor can now have current pass through.  $I_{DS} \neq 0$

- The E-field that cause the current to drift :  $E_{DS} = \frac{V_{DS}}{L}$
- Thus the drift velocity is  $v_d = \mu_n E_{DS} = \mu_n \frac{V_{DS}}{L}$
- Thus the drift current density (in  $A/m$ ) is  $J_d = Qv_d = Q_{Cap}\mu_n \frac{V_{DS}}{L}$
- Where the  $Q$  ( in  $C/m$  ) is the charge that drift in the  $n$ -channel, it comes from the charges stored in MOS capacitor  $Q_{Cap}$

Cosider the MOS capacitor  $Q_{Cap} = CV_{cap}$

The  $V_{Cap}$  is the excess voltage of  $V_{GS}$  :  $V_{Cap} = V_{GS} - V_{TN}$

$$Q_{Cap} = C (V_{GS} - V_{TN})$$

$$J_d = C (V_{GS} - V_{TN}) \mu_n \frac{V_{DS}}{L}$$

$$I = J_d W = C \mu_n \frac{W}{L} (V_{GS} - V_{TN}) V_{DS} = k_n \frac{W}{L} (V_{GS} - V_{TN}) V_{DS} \text{ ( In the S-side)}$$

$$I = J_d W = C \mu_n \frac{W}{L} (V_{GS} - V_{TN}) V_{DS} = k_n \frac{W}{L} (V_{GS} - V_{TN} - V_{DS}) V_{DS} \text{ (In the D-side)}$$

In the middle of the device, assume linear relationship, the average current

$$I_{DS} = k_n \frac{W}{L} \left( V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$$


### 2.1.3 Saturation

When  $V_{DS} = V_{GS} - V_{TN}$


$$I_{DS} = k_n \frac{W}{L} \left( V_{GS} - V_{TN} - \frac{V_{GS} - V_{TN}}{2} \right) (V_{GS} - V_{TN}) = \frac{k_n W}{2 L} (V_{GS} - V_{TN})^2 = K_n (V_{GS} - V_{TN})^2$$

## 2.2 MOSFET Circuit Operation


### 2.2.1 Cutoff

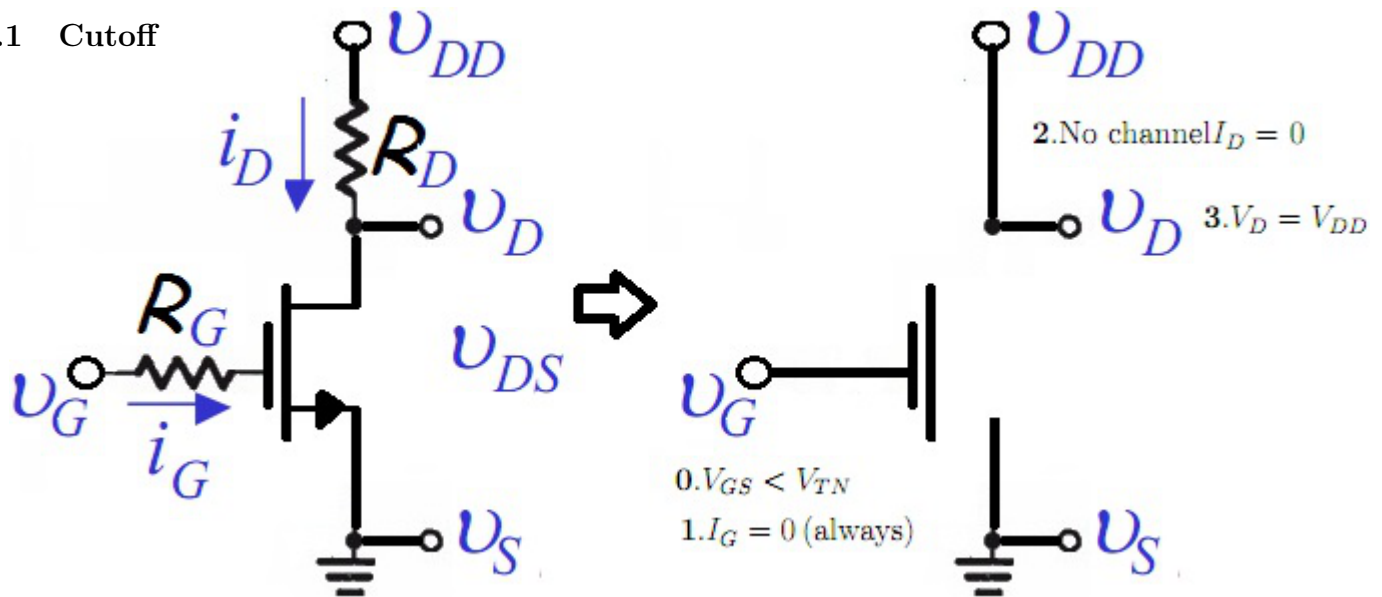

### 2.2.2 Saturation

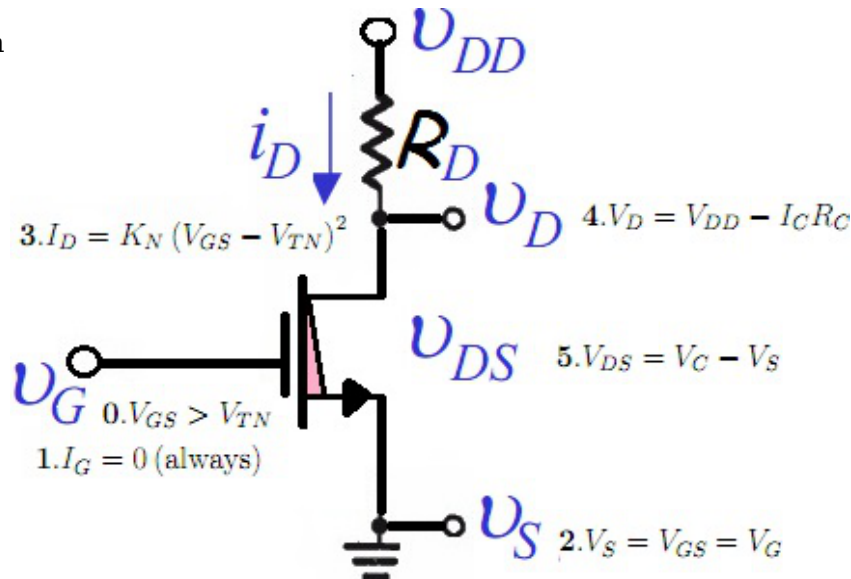

### 2.2.3 Triode / Active

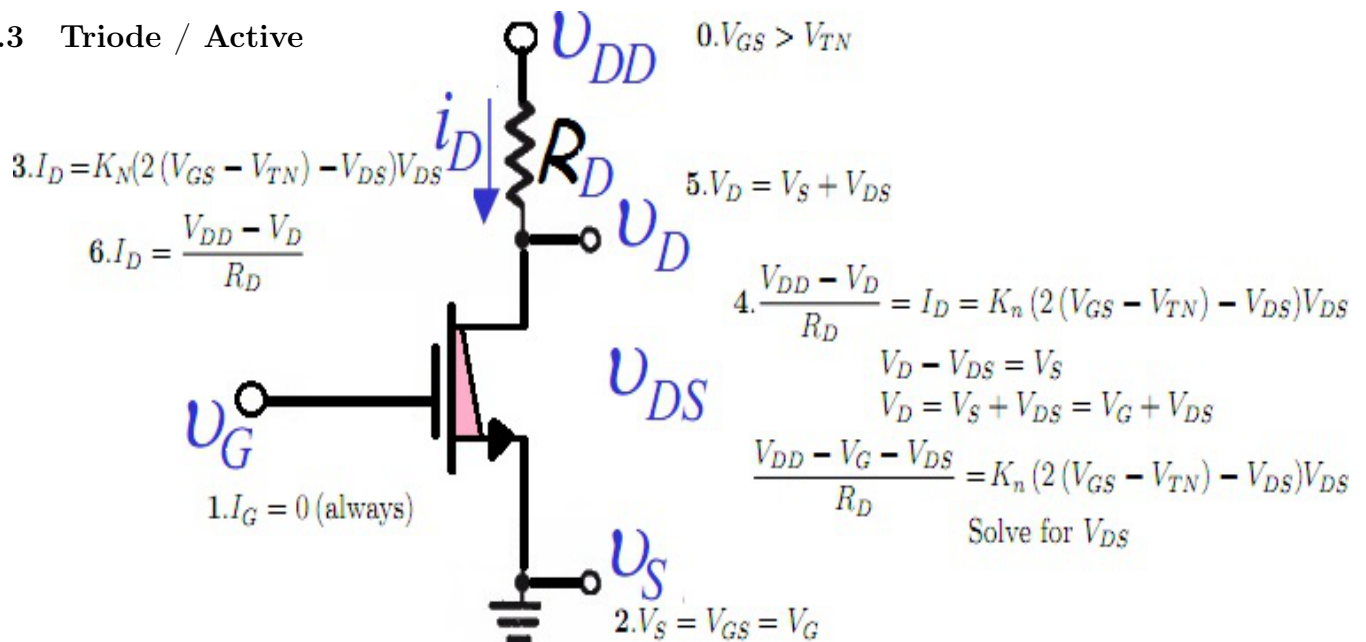

-END-