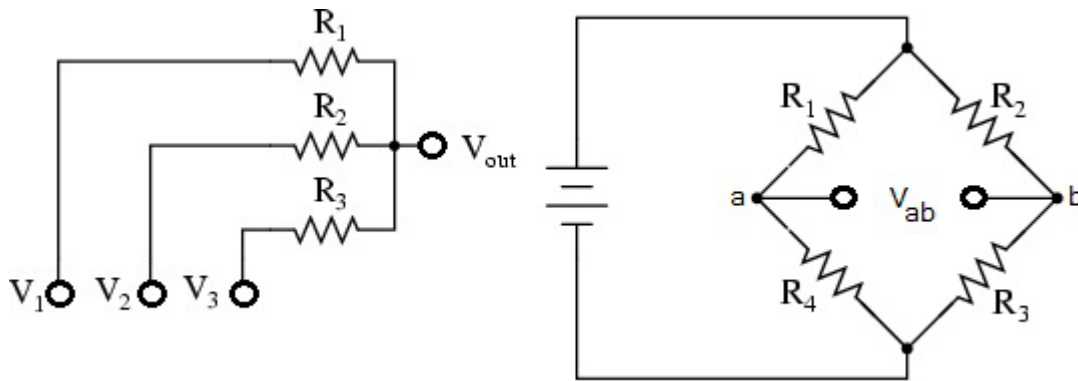


# Some Standard Electric Circuits


Ang Man Shun

2012-3-3

## Some Resistor Network



## Some OpAmp Circuits

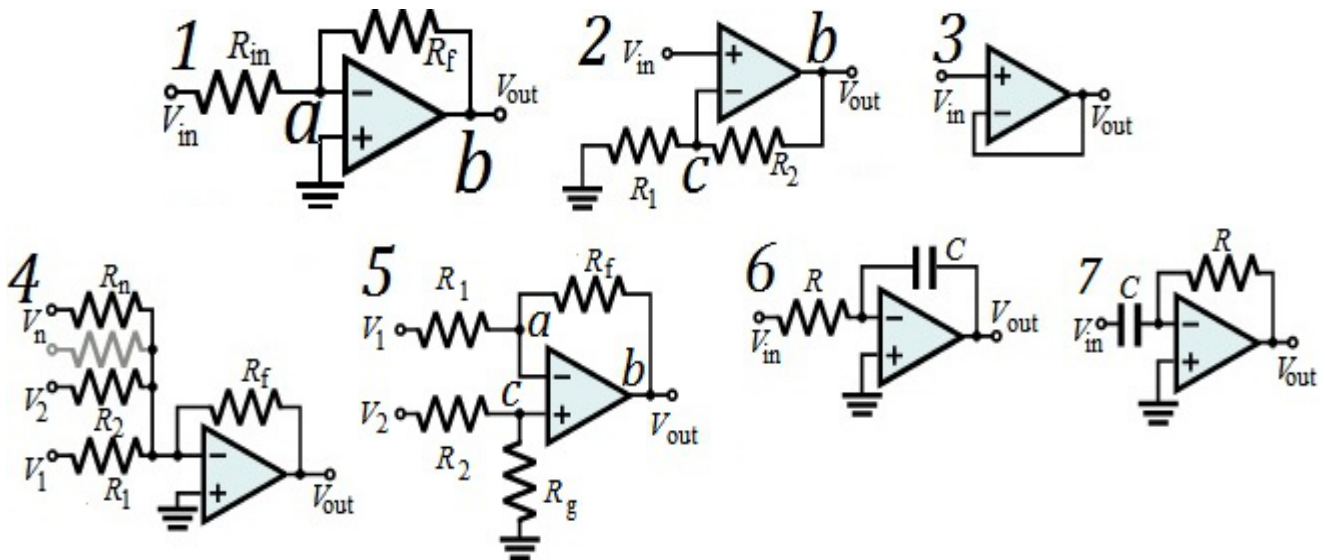

### The Virtual Short Concept for $\pm$ pins in an OpAmp

The pin  $-$  and  $+$  are virtual shorted :  $V_- = V_+$

( This is because of finite output and infinite gain of ideal OpAmp  $v_{out} = A(v_+ - v_-)$  )

Thus, when one of pin is grounded, then both pins are grounded.

# 1 The Resistor Network

## 1.1 Averager

The current of  $R_1$  is  $\frac{V_1}{R_1}$

Thus at the output point, all the current sum together :  $I_{out} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$

Since the 3 resistor is in parallel, so the equivalent resistance is  $\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)^{-1} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$

Thus the output voltage is  $I_{out} R_{eq} = \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}\right) \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)^{-1} = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$

When resistor are equal

$$R_{eq} = \frac{R}{3} \quad I_{out} = \frac{V_1 + V_2 + V_3}{R} \quad V_{out} = \frac{V_1 + V_2 + V_3}{3}$$

Generalized, for  $n$ -resistor averager The equivalent resistance is


$$R_{eq}(n) = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}\right)^{-1} = \frac{R_1 R_2 \dots R_n}{R_1 R_2 \dots R_{n-1} + R_1 R_2 \dots R_{n-2} R_n + \dots + R_2 R_3 \dots R_n}$$

$$R_{eq}(n) = \left(\sum_{i=1}^n \frac{1}{R_i}\right)^{-1} = \frac{\prod_{i=1}^n R_i}{\sum_{i=1}^n \prod_{j=1, j \neq i}^n R_j} = \frac{\text{Sum of } R \text{ taken } n \text{ at a time}}{\text{Sum of } R \text{ taken } n-1 \text{ at a time}}$$

(Analogy to Algebra of Polynomial)

The output current is  $I_{out} = \frac{V_1}{R_1} + \dots + \frac{V_n}{R_n}$

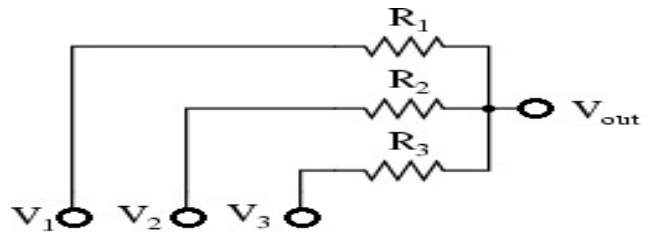And the output voltage is  $V_{out} = \frac{\frac{V_1}{R_1} + \dots + \frac{V_n}{R_n}}{\frac{1}{R_1} + \dots + \frac{1}{R_n}}$



## 1.2 Birdge

The path  $R_1 R_4$  is parallel to path  $R_2 R_3$ , thus voltage across  $R_1 + R_4$  is equal to  $R_2 + R_3$


By potential divider,  $V_a = V_{in} \frac{R_4}{R_1 + R_4}$ ,  $V_b = V_{in} \frac{R_3}{R_2 + R_3}$

Thus,  $V_{ab} = V_a - V_b = V_{in} \left(\frac{R_4}{R_1 + R_4} - \frac{R_3}{R_2 + R_3}\right)$

When  $V_{ab} = 0$ , then  $V_a = V_b$ , and thus

$$\frac{R_4}{R_1 + R_4} = \frac{R_3}{R_2 + R_3} \Rightarrow \frac{R_4}{R_1 + R_4} \frac{1/R_4} = \frac{R_3}{R_2 + R_3} \frac{1/R_3} \Rightarrow \frac{1}{\frac{R_1}{R_4} + 1} = \frac{1}{\frac{R_2}{R_3} + 1} \Rightarrow \frac{R_2}{R_3} + 1 = \frac{R_1}{R_4} + 1$$
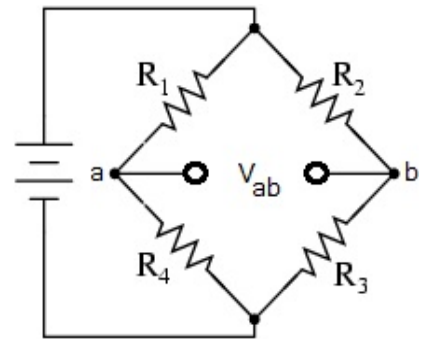
$$\Rightarrow \frac{R_1}{R_4} = \frac{R_2}{R_3}$$



## 2 OpAmp Circuits

### 2.1 Inverting Amplifier

Input current is  $I_{in} = \frac{V_{in}}{R_{in}}$


Since the  $\pm$ pin is virtual grounded ( $V_a = 0$ ), so the all current go into  $R_f$

Thus the voltage of  $R_f$  is  $V_{R_f} = I_{in}R_f = V_{in}\frac{R_f}{R_{in}}$

By KVL :  $V_a = V_{R_f} + V_b \iff 0 = V_{in}\frac{R_f}{R_{in}} + V_{out}$

Thus, the gain is  $\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$

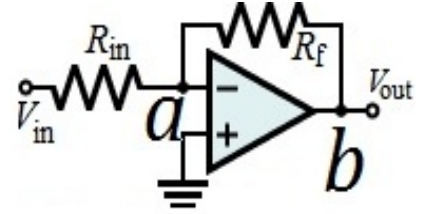When  $R_f = R_{in}$ , the OpAmp become a phase inverter ,  $V_{out} = -V_{in}$




### 2.2 Non-inverting Amplifier

Input voltage  $V_{in}$

By potential divider at point  $C$  :  $V_C = V_{out}\frac{R_1}{R_1 + R_2}$

By virtual short of  $\pm$ pin,  $V_C = V_{in}$

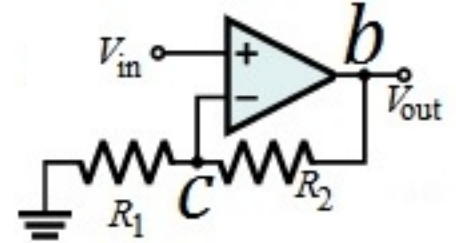So the gain is  $\frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$




### 2.3 Voltage Follower

The input voltage  $V_{in}$  equal to  $V_-$

The output voltage  $V_{out}$  equal to  $V_+$

By virtual short in  $\pm$ pin,  $V_- = V_+$

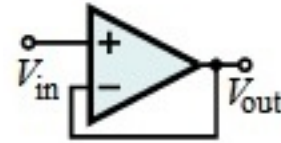Thus  $V_{out} = V_{in}$   
So the gain is  $\frac{V_{out}}{V_{in}} = 1$



### 2.4 Weighted Summer

Notice that the resistor network is an averager.

The input current of resistor  $k$  :  $I_k = \frac{V_{in,k}}{R_k}$

By KCL, the total current in node  $a$  will be  $I_a = \sum_{all k} I_k$

Since  $+$  pin is grounded, so by virtual short in  $\pm$ pin,  $-$  pin is also grounded ( $V_a = 0$ )


all current go into  $R_f$  Thus the voltage of  $R_f$  is

$$V_{R_f} = I_f R_f = I_a R_f = \left( \sum I_k \right) R_f = \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right) R_f = V_1 \frac{R_f}{R_1} + V_2 \frac{R_f}{R_2} + \dots + V_n \frac{R_f}{R_n}$$

By KVL,  $V_a = V_{R_f} + V_b \iff 0 = \left( V_1 \frac{R_f}{R_1} + V_2 \frac{R_f}{R_2} + \dots + V_n \frac{R_f}{R_n} \right) + V_{out}$

Thus  $V_{out} = - \left( V_1 \frac{R_f}{R_1} + V_2 \frac{R_f}{R_2} + \dots + V_n \frac{R_f}{R_n} \right)$

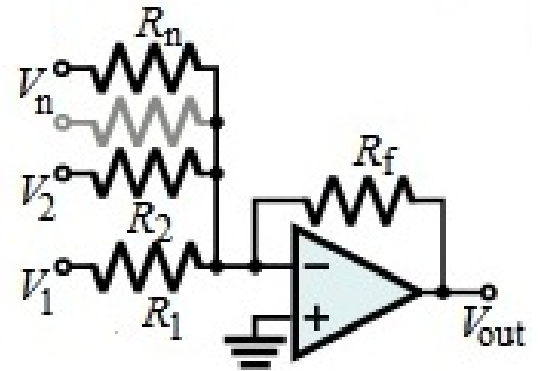If all the input voltages are equal, the gain is  $\frac{V_{out}}{V_{in}} = \frac{R_f}{R_1} + \frac{R_f}{R_2} + \dots + \frac{R_f}{R_n}$



## 2.5 Differential Amplifier

Virtual short in  $\pm$  pins, so  $V_a = V_c$ , but  $V_a, V_c \neq 0$

If  $V_1 = 0$ , this amplifier become non-inverting amplifier, At point  $C$ ,  $V_c = V_2 \frac{R_g}{R_2 + R_g}$ , this  $V_c$  is the  $V_{in}$  in non-inverting amplifier


If  $V_2 = 0$ , this amplifier become inverting amplifier, and

$$V_{out1} = -V_1 \frac{R_f}{R_1}$$

$$\text{Thus, } V_{out2} = V_c \frac{R_1 + R_f}{R_1} = V_2 \frac{R_g}{R_2 + R_g} \frac{R_1 + R_f}{R_1}$$

$$\begin{aligned} \text{The total output is } V_{out} &= V_{out1} + V_{out2} \\ &= -V_1 \frac{R_f}{R_1} + V_2 \frac{R_g}{R_2 + R_g} \frac{R_1 + R_f}{R_1} \end{aligned}$$

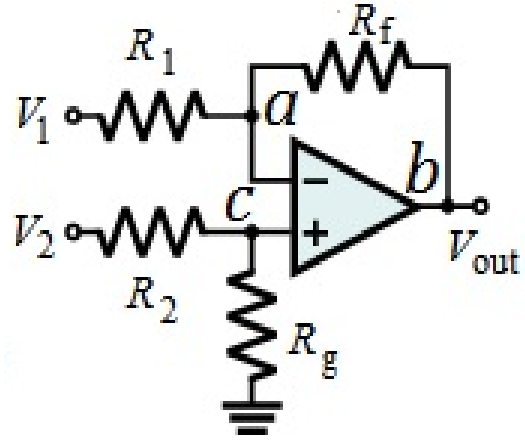For  $R_1 = R_2$ ,  $R_g = R_f$ :  $V_{out} = (V_2 - V_1) \frac{R_f}{R_1}$ , thus, the output is proportional to the difference between 2 inputs



## 2.6 Integrator

The input current is  $I_{in} = \frac{V_{in}}{R}$

Since + pin is GND and virtual short of  $\pm$  pin,  $V_a = 0$ , so all current goes into the capacitor


Capacitor charge-capacitance-voltage relation is :  $Q_{cap} = V_{cap}C$

$$\text{Thus } I_{cap} = \frac{dQ_{cap}}{dt} = C \frac{dV_{cap}}{dt}$$

$$I_{in} = I_{cap} \iff \frac{V_{in}}{R} = C \frac{dV_{cap}}{dt} \iff V_{cap} = \frac{1}{RC} \int_0^t V_{in} dt, \text{ assume } V_{cap}(t=0) = 0$$

$$\text{By KVL : } V_a = V_{Cap} + V_b \iff 0 = V_{cap} + V_{out} \iff V_{out} = -V_{cap}$$
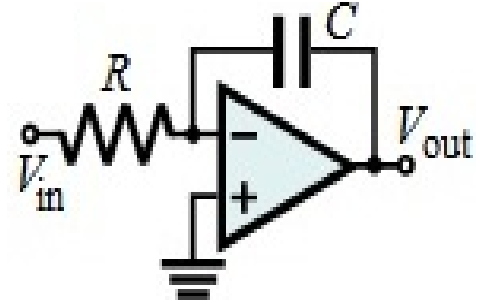
$$\text{Thus } V_{out} = \frac{-1}{RC} \int_0^t V_{in} dt$$



## 2.7 Differentiator

The capacitor equation :  $Q_{cap} = CV_{cap}$

$$\implies I_{cap} = \frac{dQ_{cap}}{dt} = C \frac{dV_{cap}}{dt} = C \frac{dV_{in}}{dt}$$

By +pin GND &  $\pm$ pin virtual short,  $I_R = I_{cap}$

$$\implies V_R = CR \frac{dV_{in}}{dt}$$

$$\text{By KCL : } V_a = V_R + V_b \iff 0 = RC \frac{dV_{in}}{dt} + V_{out}$$

$$V_{out} = RC \frac{dV_{in}}{dt}$$

*Remark.* If the input is  $A \sin \omega t$ , then output is  $\omega A \cos \omega t$ , thus the output will have a larger amplitude for high frequency component. Thus differentiator will also amplify the high frequency noise.

